

课程名称：EDA 技术综合设计

设计报告名称：设计三 二进制转换十进制

班级：通信 214

姓名：王峤宇

学号：214022

一、设计内容及原理

数码管设计

利用视觉暂留, 采用动态扫描显示方式完成数码管设计, 每个数码管包括 7 个 LED 管和 1 个小圆点, 通过 8 个 IO 口控制一位数码管显示, 通过分时复用的扫描显示方案进行数码管驱动可以有效地提高对 IO 口资源的利用。板上提供的数码管为共阴极数码管。

二进制转十进制 BCD 码

读取拨码开关输入的二进制后, 通过逐位移位法的方式, 四位二进制数据装换成两个 4 位的 BCD 码保存。

基础任务

设计任务: 完成 4 位二进制整数转成十进制数, 输入由拨码开关给, 输出由数码管显示。

提高内容

设计任务: 完成 4 位二进制纯小数转成十进制数, 输入由拨码开关给, 输出由数码管显示。

小数部分的设计较为困难, 但输入仅有 4 位二进制, 直接采用 case 语句完成所有情况的小数输出即可。

拓展任务

任务要求: 完成 8 位二进制实数转成十进制数 (其中四位整数, 四位小数), 输入由拨码开关给, 输出由数码管显示。

将前两部分任务设计的模块进行整合, 八位拨码开关, 分别作为四位整数输入和四位小数输入, 数码管两位用于整数输出, 四位用于小数部分输出。

最终设计得到的 8 位二进制实数转十进制整数的模块框图如图 1 所示。

 


图 1: 实数二进制转十进制模块框图

二、设计过程

基础任务

通过逐位移位法实现的四位无符号数转化为 BCD 码的源文件如下:

Listing 1: 二进制转 BCD

```
1 module int2bcd_4bit(  
2     input  [3:0] uint4,  
3     output [3:0] outBCD0,  
4     output [3:0] outBCD1  
5 );  
6 reg [11:0] bcd_r0, bcd_r1, bcd_r2;  
7  
8 /* 直接移位两次 */  
9 always @(*) begin  
10     bcd_r0 = {6'b0, uint4, 2'b0};  
11 end  
12  
13 /* 移位第三次结果 */  
14 always @(*) begin  
15     bcd_r1 = {bcd_r0[10:0], 1'b0};  
16     if (bcd_r1[7:4] > 4'b0100) bcd_r1[7:4] = bcd_r1[7:4] + 4'b0011;  
17 end  
18  
19 /* 移位四次结果 */  
20 always @(*) begin  
21     bcd_r2 = {bcd_r1[10:0], 1'b0};  
22 end  
23  
24 /* 输出结果 */  
25 assign outBCD0 = bcd_r2[7:4];  
26 assign outBCD1 = bcd_r2[11:8];  
27 endmodule
```

时序扫描完成的数码管显示源文件如下, 以四个数码管为单位构建模块:

Listing 2: 数码管扫描显示

```
1 module scan_led_hex_disp_4(  
2     input clk, rst,          /* 100MHz 时钟与复位 */  
3     input [3:0] hex0, hex1, hex2, hex3, /* 显存 */  
4     input [3:0] dp,          /* 小数点 */  
5     output reg [3:0] an,      /* 片选信号 */  
6     output reg [7:0] sseg     /* 八段数码管接口 */  
7 );  
8  
9 localparam N = 16 + 2; /* 100MHz 时钟分频, 100Mhz/ 2^16 */  
10 reg [N-1:0] regN;  
11  
12 always @(posedge clk, posedge rst) begin  
13     if (rst) /* 异步, 高电平复位 */
```

```

14         regN <= 0;
15     else
16         regN <= regN + 1;
17     end
18
19     always @(*) begin        /* 时分复用 */
20         case (regN[N-1:N-2])
21             2'b00: begin
22                 an <= 4'b0001;
23                 sseg[6:0] <= dt_translate(hex0);
24                 sseg[7] <= dp[3];
25             end
26             2'b01: begin
27                 an <= 4'b0010;
28                 sseg[6:0] <= dt_translate(hex1);
29                 sseg[7] <= dp[2];
30             end
31             2'b10: begin
32                 an <= 4'b0100;
33                 sseg[6:0] <= dt_translate(hex2);
34                 sseg[7] <= dp[1];
35             end
36             2'b11: begin
37                 an <= 4'b1000;
38                 sseg[6:0] <= dt_translate(hex3);
39                 sseg[7] <= dp[0];
40             end
41         endcase
42     end
43
44     function [6:0] dt_translate;    /* 数码管译码函数 */
45     input [3:0] data;
46     begin
47         case(data)
48             4'd0: dt_translate = 7'b1111110;    //number 0 -> 0x7e
49             4'd1: dt_translate = 7'b0110000;    //number 1 -> 0x30
50             4'd2: dt_translate = 7'b1101101;    //number 2 -> 0x6d
51             4'd3: dt_translate = 7'b1111001;    //number 3 -> 0x79
52             4'd4: dt_translate = 7'b0110011;    //number 4 -> 0x33
53             4'd5: dt_translate = 7'b1011011;    //number 5 -> 0x5b
54             4'd6: dt_translate = 7'b1011111;    //number 6 -> 0x5f
55             4'd7: dt_translate = 7'b1110000;    //number 7 -> 0x70
56             4'd8: dt_translate = 7'b1111111;    //number 8 -> 0x7f
57             4'd9: dt_translate = 7'b1111011;    //number 9 -> 0x7b
58         endcase
59     end
60     endfunction
61 endmodule

```

整体系统的 top 文件如下:

Listing 3: top 文件

```

1 module bin2dec_top(
2     input clk,                /* 100MHz */
3     input rst,                /* 高电平异步复位 */
4     input [7:0] real_bin,     /* 输入的四位整数加四位小数的二进制实数 */
5     output [7:0] sseg1, sseg2, /* 八段数码管 */
6     output [3:0] an1, an2     /* 片选信号 */
7 );
8
9 /* 计算整数部分的BCD码 */
10 wire [3:0] bcd_int0, bcd_int1;
11 int2bcd_4bit int2bcd_4bit_inst (
12     .uint4(real_bin[7:4]),
13     .outBCD0(bcd_int0),
14     .outBCD1(bcd_int1)
15 );
16
17 /* 第一个四数码管显示整数部分 */
18 scan_led_hex_disp_4 scan_led_hex_disp_4_inst_0 (
19     .clk(clk), .rst(rst),
20     .hex0(4'b0000), .hex1(4'b0000), .hex2(bcd_int1), .hex3(bcd_int0), .dp(4'b0001),
21     .an(an1), .sseg(sseg1)
22 );
23
24 scan_led_hex_disp_4 scan_led_hex_disp_4_inst_1 (
25     .clk(clk), .rst(rst),
26     .hex0(4'b0000), .hex1(4'b0000), .hex2(4'b0000), .hex3(4'b0000), .dp(4'b0000),
27     .an(an2), .sseg(sseg2)
28 );
29 endmodule

```

仿真文件如下:

Listing 4: 整数部分仿真文件

```

1 module bin2dec_top_tb;
2     reg clk;
3     reg rst;
4     reg [7:0] real_bin;
5     wire [7:0] sseg1, sseg2;
6     wire [3:0] an1, an2;
7
8     initial begin
9         clk = 0;
10        rst = 1;
11        #10;
12        clk = 1;
13        #10;
14        rst = 0;
15        real_bin = 8'b0;
16        forever begin
17            #100;

```

```

18     real_bin = real_bin + 8'b0001_0000;
19     if (real_bin == 8'b0) begin
20         $finish;
21     end
22 end
23 end
24 /* 生成时钟 */
25 always @(*) #5 clk <= ~clk;
26 /* 例化top */
27 bin2dec_top bin2dec_top_inst (
28     .clk(clk),
29     .rst(rst),
30     .real_bin(real_bin),
31     .sseg1(sseg1),
32     .sseg2(sseg2),
33     .an1(an1),
34     .an2(an2)
35 );
36 endmodule

```

提高任务

浮点数设计较为复杂, 但由于输入位数较少, 通过 case 语句实现, 实现源文件如下:

Listing 5: 二进制小数转十进制

```

1 module float2bcd_4bit(
2     input [3:0] float4,
3     output [3:0] BCD0, BCD1, BCD2, BCD3
4 );
5     reg [3:0] BCD0_r, BCD1_r, BCD2_r, BCD3_r;
6
7     always @(*) begin
8         case (float4)
9             4'b0000: {BCD0_r, BCD1_r, BCD2_r, BCD3_r} = 16'b0; // 0.0000
10            4'b0001: {BCD0_r, BCD1_r, BCD2_r, BCD3_r} = {4'd0, 4'd6, 4'd2, 4'd5}; // 0.0625
11            4'b0010: {BCD0_r, BCD1_r, BCD2_r, BCD3_r} = {4'd1, 4'd2, 4'd5, 4'd0}; // 0.125
12            4'b0011: {BCD0_r, BCD1_r, BCD2_r, BCD3_r} = {4'd1, 4'd8, 4'd7, 4'd5}; // 0.1875
13            4'b0100: {BCD0_r, BCD1_r, BCD2_r, BCD3_r} = {4'd2, 4'd5, 4'd0, 4'd0}; // 0.25
14            4'b0101: {BCD0_r, BCD1_r, BCD2_r, BCD3_r} = {4'd3, 4'd1, 4'd2, 4'd5}; // 0.3125
15            4'b0110: {BCD0_r, BCD1_r, BCD2_r, BCD3_r} = {4'd3, 4'd7, 4'd5, 4'd0}; // 0.375
16            4'b0111: {BCD0_r, BCD1_r, BCD2_r, BCD3_r} = {4'd4, 4'd3, 4'd7, 4'd5}; // 0.4375
17            4'b1000: {BCD0_r, BCD1_r, BCD2_r, BCD3_r} = {4'd5, 4'd0, 4'd0, 4'd0}; // 0.5
18            4'b1001: {BCD0_r, BCD1_r, BCD2_r, BCD3_r} = {4'd5, 4'd6, 4'd2, 4'd5}; // 0.5625
19            4'b1010: {BCD0_r, BCD1_r, BCD2_r, BCD3_r} = {4'd6, 4'd2, 4'd5, 4'd0}; // 0.625
20            4'b1011: {BCD0_r, BCD1_r, BCD2_r, BCD3_r} = {4'd6, 4'd8, 4'd7, 4'd5}; // 0.6875
21            4'b1100: {BCD0_r, BCD1_r, BCD2_r, BCD3_r} = {4'd7, 4'd5, 4'd0, 4'd0}; // 0.75
22            4'b1101: {BCD0_r, BCD1_r, BCD2_r, BCD3_r} = {4'd8, 4'd1, 4'd2, 4'd5}; // 0.8125
23            4'b1110: {BCD0_r, BCD1_r, BCD2_r, BCD3_r} = {4'd8, 4'd7, 4'd5, 4'd0}; // 0.875
24            4'b1111: {BCD0_r, BCD1_r, BCD2_r, BCD3_r} = {4'd9, 4'd3, 4'd7, 4'd5}; // 0.9375
25            default: {BCD0_r, BCD1_r, BCD2_r, BCD3_r} = {4'd0, 4'd0, 4'd0, 4'd0}; // Default case

```

```

26         endcase
27     end
28
29     assign BCD0 = BCD0_r;
30     assign BCD1 = BCD1_r;
31     assign BCD2 = BCD2_r;
32     assign BCD3 = BCD3_r;
33 endmodule

```

修改后的 top 源文件新增内容如下:

Listing 6: 添加小数部分的 Top 文件修改内容

```

1  /* 计算小数部分的BCD码 */
2  wire [3:0] bcd_float0, bcd_float1, bcd_float2, bcd_float3;
3  float2bcd_4bit float2bcd_4bit_inst (
4      .float4(real_bin[3:0]),
5      .BCD0(bcd_float0), .BCD1(bcd_float1),
6      .BCD2(bcd_float2), .BCD3(bcd_float3)
7  );
8  scan_led_hex_disp_4 scan_led_hex_disp_4_inst_1 (
9      .clk(clk), .rst(rst),
10     .hex0(bcd_float0), .hex1(bcd_float1), .hex2(bcd_float2), .hex3(bcd_float3), .dp(4'b0000),
11     .an(an2), .sseg(sseg2)
12 );

```

对应的仿真文件的更改部分如下, 将激励改为遍历小数部分测试, 并且不再对数码管输出进行仿真测试, 直接测试小数输出 bcd 是否正确:

Listing 7: 小数转十进制仿真文件

```

1  initial begin
2      clk = 0;
3      rst = 1;
4      #10;
5      clk = 1;
6      #10;
7      rst = 0;
8      real_bin = 8'b0;
9      forever begin
10         #100;
11         real_bin = real_bin + 8'b0000_0001; /* 遍历浮点数情况 */
12         if (real_bin[3:0] == 4'b0) begin
13             $finish;
14         end
15     end
16 end

```

拓展任务

模块整合后的源文件如下:

Listing 8: 最终 top 源文件

```

1 module bin2dec_top(
2     input clk,                /* 100MHz */
3     input rst,                /* 高电平异步复位 */
4     input [7:0] real_bin,      /* 输入的四位整数加四位小数的二进制实数 */
5     output [7:0] sseg1, sseg2, /* 八段数码管 */
6     output [3:0] an1, an2      /* 片选信号 */
7 );
8
9 /* 计算整数部分的BCD码 */
10 wire [3:0] bcd_int0, bcd_int1;
11 int2bcd_4bit int2bcd_4bit_inst (
12     .uint4(real_bin[7:4]),
13     .outBCD0(bcd_int0),
14     .outBCD1(bcd_int1)
15 );
16
17 /* 第一个四数码管显示整数部分 */
18 scan_led_hex_disp_4 scan_led_hex_disp_4_inst_0 (
19     .clk(clk), .rst(rst),
20     .hex0(4'b0000), .hex1(4'b0000), .hex2(bcd_int1), .hex3(bcd_int0), .dp(4'b0001),
21     .an(an1), .sseg(sseg1)
22 );
23
24 /* 计算小数部分的BCD码 */
25 wire [3:0] bcd_float0, bcd_float1, bcd_float2, bcd_float3;
26 float2bcd_4bit float2bcd_4bit_inst (
27     .float4(real_bin[3:0]),
28     .BCD0(bcd_float0), .BCD1(bcd_float1),
29     .BCD2(bcd_float2), .BCD3(bcd_float3)
30 );
31 scan_led_hex_disp_4 scan_led_hex_disp_4_inst_1 (
32     .clk(clk), .rst(rst),
33     .hex0(bcd_float0), .hex1(bcd_float1), .hex2(bcd_float2), .hex3(bcd_float3), .dp(4'b0000),
34     .an(an2), .sseg(sseg2)
35 );
36 endmodule

```

仿真文件中的更改后的激励如下, 实现对所有可能输入数据的遍历:

Listing 9: 系统仿真激励

```

1 initial begin
2     clk = 0;
3     rst = 1;
4     #10;
5     clk = 1;
6     #10;
7     rst = 0;
8     real_bin = 8'b0;
9     forever begin
10        #100;

```



```

11     real_bin = real_bin + 8'b0000_0001; /* 遍历浮点数情况 */
12     if (real_bin == 8'b0) begin
13         $finish;
14     end
15 end
16 end

```

本系统设计最终需要用到，八个数码管，其中数码管为共阴极，由三极管驱动，整个系统的约束文件下：

Listing 10: 系统约束文件

```

1  set_property IOSTANDARD LVCMOS33 [get_ports clk]
2  set_property IOSTANDARD LVCMOS33 [get_ports rst]
3  set_property PACKAGE_PIN P17 [get_ports clk]
4  set_property PACKAGE_PIN R11 [get_ports rst]
5  set_property IOSTANDARD LVCMOS33 [get_ports {real_bin[7]}]
6  set_property IOSTANDARD LVCMOS33 [get_ports {real_bin[6]}]
7  set_property IOSTANDARD LVCMOS33 [get_ports {real_bin[5]}]
8  set_property IOSTANDARD LVCMOS33 [get_ports {real_bin[4]}]
9  set_property IOSTANDARD LVCMOS33 [get_ports {real_bin[3]}]
10 set_property IOSTANDARD LVCMOS33 [get_ports {real_bin[2]}]
11 set_property IOSTANDARD LVCMOS33 [get_ports {real_bin[1]}]
12 set_property IOSTANDARD LVCMOS33 [get_ports {real_bin[0]}]
13 set_property IOSTANDARD LVCMOS33 [get_ports {sseg1[7]}]
14 set_property IOSTANDARD LVCMOS33 [get_ports {sseg1[6]}]
15 set_property IOSTANDARD LVCMOS33 [get_ports {sseg1[5]}]
16 set_property IOSTANDARD LVCMOS33 [get_ports {sseg1[4]}]
17 set_property IOSTANDARD LVCMOS33 [get_ports {sseg1[3]}]
18 set_property IOSTANDARD LVCMOS33 [get_ports {sseg1[2]}]
19 set_property IOSTANDARD LVCMOS33 [get_ports {sseg1[1]}]
20 set_property IOSTANDARD LVCMOS33 [get_ports {sseg1[0]}]
21 set_property IOSTANDARD LVCMOS33 [get_ports {sseg2[7]}]
22 set_property IOSTANDARD LVCMOS33 [get_ports {sseg2[6]}]
23 set_property IOSTANDARD LVCMOS33 [get_ports {sseg2[5]}]
24 set_property IOSTANDARD LVCMOS33 [get_ports {sseg2[4]}]
25 set_property IOSTANDARD LVCMOS33 [get_ports {sseg2[3]}]
26 set_property IOSTANDARD LVCMOS33 [get_ports {sseg2[2]}]
27 set_property IOSTANDARD LVCMOS33 [get_ports {sseg2[1]}]
28 set_property IOSTANDARD LVCMOS33 [get_ports {sseg2[0]}]
29 set_property IOSTANDARD LVCMOS33 [get_ports {an1[3]}]
30 set_property IOSTANDARD LVCMOS33 [get_ports {an1[2]}]
31 set_property IOSTANDARD LVCMOS33 [get_ports {an1[1]}]
32 set_property IOSTANDARD LVCMOS33 [get_ports {an1[0]}]
33 set_property IOSTANDARD LVCMOS33 [get_ports {an2[3]}]
34 set_property IOSTANDARD LVCMOS33 [get_ports {an2[2]}]
35 set_property IOSTANDARD LVCMOS33 [get_ports {an2[1]}]
36 set_property IOSTANDARD LVCMOS33 [get_ports {an2[0]}]
37 set_property PACKAGE_PIN P5 [get_ports {real_bin[7]}]
38 set_property PACKAGE_PIN P4 [get_ports {real_bin[6]}]
39 set_property PACKAGE_PIN P3 [get_ports {real_bin[5]}]
40 set_property PACKAGE_PIN P2 [get_ports {real_bin[4]}]

```

```

41 set_property PACKAGE_PIN R2 [get_ports {real_bin[3]}]
42 set_property PACKAGE_PIN M4 [get_ports {real_bin[2]}]
43 set_property PACKAGE_PIN N4 [get_ports {real_bin[1]}]
44 set_property PACKAGE_PIN R1 [get_ports {real_bin[0]}]
45 set_property PACKAGE_PIN G2 [get_ports {an1[0]}]
46 set_property PACKAGE_PIN C2 [get_ports {an1[1]}]
47 set_property PACKAGE_PIN C1 [get_ports {an1[2]}]
48 set_property PACKAGE_PIN H1 [get_ports {an1[3]}]
49 set_property PACKAGE_PIN G6 [get_ports {an2[3]}]
50 set_property PACKAGE_PIN E1 [get_ports {an2[2]}]
51 set_property PACKAGE_PIN F1 [get_ports {an2[1]}]
52 set_property PACKAGE_PIN G1 [get_ports {an2[0]}]
53 set_property PACKAGE_PIN D5 [get_ports {sseg1[7]}]
54 set_property PACKAGE_PIN B4 [get_ports {sseg1[6]}]
55 set_property PACKAGE_PIN A4 [get_ports {sseg1[5]}]
56 set_property PACKAGE_PIN A3 [get_ports {sseg1[4]}]
57 set_property PACKAGE_PIN B1 [get_ports {sseg1[3]}]
58 set_property PACKAGE_PIN A1 [get_ports {sseg1[2]}]
59 set_property PACKAGE_PIN B3 [get_ports {sseg1[1]}]
60 set_property PACKAGE_PIN B2 [get_ports {sseg1[0]}]
61 set_property PACKAGE_PIN H2 [get_ports {sseg2[7]}]
62 set_property PACKAGE_PIN D4 [get_ports {sseg2[6]}]
63 set_property PACKAGE_PIN E3 [get_ports {sseg2[5]}]
64 set_property PACKAGE_PIN D3 [get_ports {sseg2[4]}]
65 set_property PACKAGE_PIN F4 [get_ports {sseg2[3]}]
66 set_property PACKAGE_PIN F3 [get_ports {sseg2[2]}]
67 set_property PACKAGE_PIN E2 [get_ports {sseg2[1]}]
68 set_property PACKAGE_PIN D2 [get_ports {sseg2[0]}]

```

三、仿真结果

基础任务

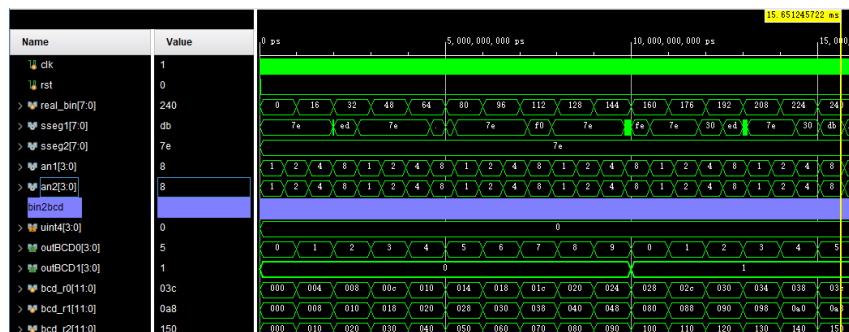


图 2: 整数部分仿真结果

对整数部分和数码管显示的仿真如图 2所示, 仿真文件中控制每 1ms 控制输入的实数数据自增, 整数部分从 0 自增到 15, 相应的 BCD 码输出正确。显示部分扫描四个数码管的片选步进为 100MHz

的 216 分频, 大概在 1.5KHz 左右, 0.6ms。可以通过时序图看到随着片选信号的改变, 数码管的输出也在随着改变。

提高任务

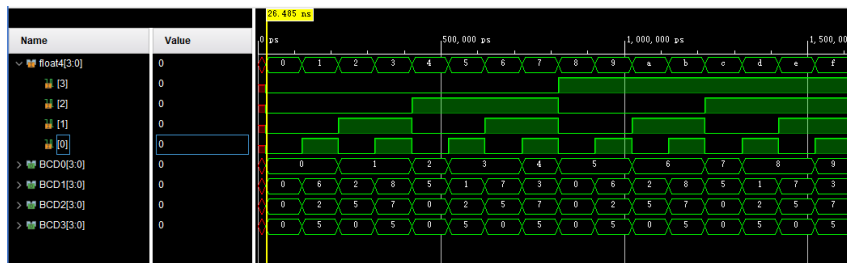


图 3: 小数部分仿真结果

对小数部分的仿真如图 2所示, 仿真文件中控制每 100ns 控制输入的实数小数部分数据自增, 小数部分的数据从 0000 到 1111, 对应数据从 0000 到 0.9375, 对应仿真图中数据为 16 进制显示, 可以看到对应的 4 个 BCD 码从 0000 增加到 9375, 对小数部分的 BCD 码解析输出无误。

拓展任务

 


图 4: 实数设计仿真结果

对最终的实数设计的仿真如图 4所示, 仿真文件中控制每 100ns 控制输入的实数数据自增, 每次增加 0.0625, 实数的数据从 00000000 到 11111111, 对应数据从 0 到 15.9375, 对应仿真图中数据输入实数改为小数模式, 由于仿真窗口限制, 仅展示部分结果, 可以看到对应的十进制小数 (二进制存储状态) 被转化成六个 BCD 码, 并一一对应, 准确无误。

四、硬件验证结果

基础任务

 


图 5: 整数部分硬件验证

针对整数部分的数码管的二进制转十进制硬件验证结果如图 5所示, 其中拨码开关从左开始数的高四位作为整数部分的输出, 由图中标注可以得到, 当输入为 4'b1101 时, 对应的十进制数是 13, 显示成功, 并且显示由小数点用于区分整数和小数。

提高任务

 


图 6: 小数部分硬件验证

针对小数部分的数码管的二进制转十进制硬件验证结果如图 6所示, 其中拨码开关从左开始数的后四个作为二进制小数部分的输入, 由图中标注可以得到, 当输入为.1001 时, 输出的十进制小数部分为.5625, .0110 时输出为.3750, 以.0110 为例, 输出为

$$.0110 : 0 * 2^{-1} + 1 * 2^{-2} + 1 * 2^{-3} + 0 * 2^{-4} = 0.3750$$

拓展任务

 


图 7: 八位实数硬件验证

针对小数部分的数码管的二进制转十进制硬件验证结果如图 7所示。

五、问题解决

设计初期, 对二进制转十进制的硬件实现思路不了解

解决: 通过查阅资料, 了解了二进制码转 BCD 码的逐位移位法, 并且在设计过程中对四位的逐位移位计算过程进行了一定的优化, 可以得到结论, 对于四位二进制转化为 BCD 码的过程中, 仅需要一次判断大四加三即可, 通过 wire 实现级间缓冲, 利用组合逻辑描述实现类似时序逻辑数据处理的效果。

在设计组合逻辑的时候 assign 语句难以实现复杂逻辑描述

解决: 对于 wire 等线网类型数据, 无法在 always 语句块中赋值, 无法直接使用 if 或者 case 等条件分支语句块, 只能使用简单的问号表达式, 通常在实现复杂组合逻辑时可以先声明相应的 reg 类型变量, 在 always 语句块中完成组合逻辑设计, 最后再通过 assign 语句将相应的 reg 数据赋值给 wire 线网类型。

六、心得体会

如果不考虑数码管显示的话,本次实验与实验二同样是进行组合逻辑电路设计,但可以明显感受到难度的上升,本次电路设计过程中,主要的难点在于二进制整数转化为BCD码和二进制小数转化为BCD码的实现,由于本次设计过程中,只需要考虑4位二进制的BCD码输出,其仅仅相当于4位输入的组组合逻辑电路,最终得到的综合工具会对其优化,难点主要在于如何用Verilog语句描述该过程,比如Verilog中循环语句对于二进制转BCD的逐位移位法很有效,虽然for循环有着与C语言相同的语法风格,但for循环并不存在对应的实际电路,综合工具有可能会将for的循环体视作一个模块,然后综合时很有可能生成循环次数个模块,也有可能通过优化直接将for循环实现的功能用其他电路替代,需要谨慎使用。